

Figure A03.1 - Driving a Solenoid Or Light

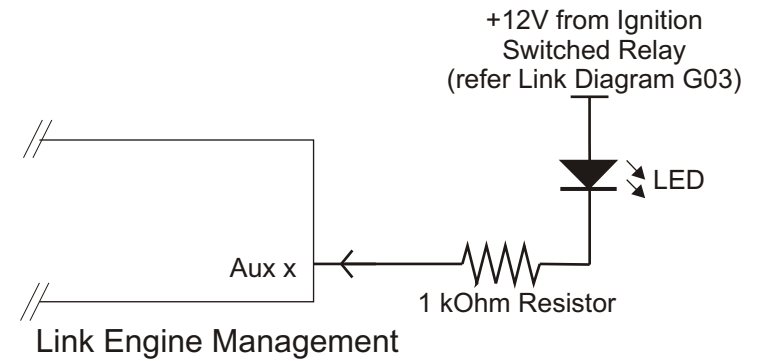


Figure A03.1 - Driving a LED

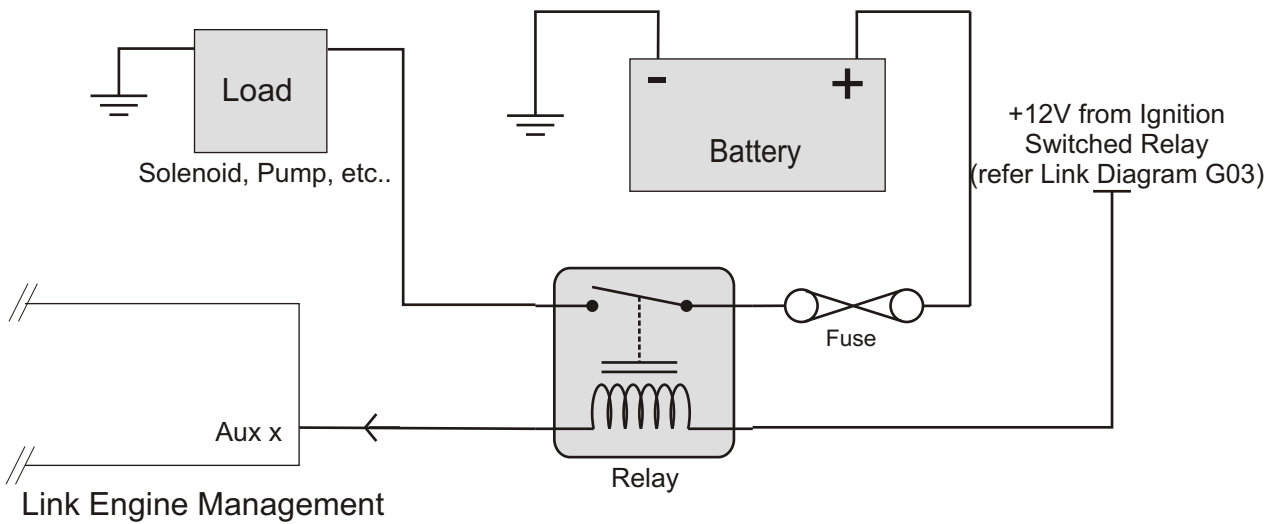


Figure A03.2 - Driving a Relay